

Assignment 3 – Diode Applications

---

**Question 1:**

(a) Thermal voltage  $V_T$  at 25°C

The thermal voltage is calculated by the formula:

$$V_T = \frac{kT}{q}$$

where

- $k = 1.38 \times 10^{-23}$  J/K (Boltzmann constant)
- $q = 1.6 \times 10^{-19}$  C (electron charge)
- $T$  is the temperature in Kelvin

**Step 1: Convert temperature to Kelvin**

$$T = 25 + 273 = 298 \text{ K}$$

**Step 2: Substitute values**

$$V_T = \frac{1.38 \times 10^{-23} \times 298}{1.6 \times 10^{-19}}$$
$$V_T \approx 0.0257 \text{ V}$$

(b) Diode current  $I_D$

Given:

- $I_S = 40 \text{ nA}$
- $n = 2$
- $V_D = 0.5 \text{ V}$

The diode current equation is:

$$I_D = I_S \left( e^{\frac{V_D}{nV_T}} - 1 \right)$$

**Step 1: Calculate  $nV_T$**

$$nV_T = 2 \times 0.0257 = 0.0514 \text{ V}$$

**Step 2: Calculate the exponent**

$$\frac{V_D}{nV_T} = \frac{0.5}{0.0514} \approx 9.73$$

**Step 3: Calculate the current**

$$I_D = 40 \times 10^{-9}(e^{9.73} - 1)$$
$$I_D \approx 6.70 \times 10^{-4} \text{ A}$$

**Question 2: Chapter 2 - Problem 4 (Boylestad)**

- Supply voltage  $E = 30 \text{ V}$

- Resistor  $R = 1.5 \text{ k}\Omega$

- Silicon diode

(a) Approximate diode model

For a silicon diode, the forward voltage is assumed to be:

$$V_D \approx 0.7 \text{ V}$$

**Step 1: Apply KVL**

$$E = V_D + V_R$$
$$V_R = 30 - 0.7 = 29.3 \text{ V}$$

**Step 2: Calculate diode current**

$$I_D = \frac{V_R}{R} = \frac{29.3}{1500}$$
$$I_D \approx 19.53 \text{ mA}$$

(b) Ideal diode model

For an ideal diode, the forward voltage drop is:

$$V_D = 0 \text{ V}$$

**Step 1: Voltage across resistor**

$$V_R = 30 \text{ V}$$

**Step 2: Diode current**

$$I_D = \frac{30}{1500} = 20 \text{ mA}$$

(c) Comparison

The current using the approximate model is  $19.53 \text{ mA}$ ,  
and using the ideal model is  $20 \text{ mA}$ .

The difference is small (about 2.35%), so the ideal model gives a reasonable result when the supply voltage is much larger than the diode voltage drop.

### **Question 3: Chapter 2 - Problem 5 (Boylestad)**

Assume silicon diodes with forward voltage:

$$V_D \approx 0.7 \text{ V}$$

(a)

The diode is reverse biased, so it does not conduct.

$$I = 0$$

(b)

Both diodes are forward biased and conduct.

#### **Step 1: Voltage after diode**

$$V = -20 + 0.7 = -19.3 \text{ V}$$

#### **Step 2: Current through each resistor**

For  $10\Omega$ :

$$I_{10} = \frac{0 - (-19.3)}{10} = 1.93 \text{ A}$$

For  $20\Omega$ :

$$I_{20} = \frac{0 - (-19.3)}{20} = 0.965 \text{ A}$$

#### **Step 3: Total current**

$$I = I_{10} + I_{20} = 2.895 \text{ A}$$

(c)

The middle branch has two opposite diodes, so no current flows in that branch.

Only the  $10\Omega$  resistor conducts.

$$I = \frac{10}{10} = 1\text{ A}$$

#### **Question 4: Chapter 2 – Problem 11 (Boylestad)**

(a)

**Step 1: Output voltage**

$$V_o = 1 - 0.7 = 0.3\text{ V}$$

**Step 2: Current**

$$I = \frac{0.3}{1000} = 0.3\text{ mA}$$

(b)

**Step 1: Total supply voltage**

$$V = 16 - (-4) = 20\text{ V}$$

**Step 2: Voltage across resistor**

$$V_R = 20 - 1.4 = 18.6\text{ V}$$

**Step 3: Current**

$$I = \frac{18.6}{4700} \approx 3.96\text{ mA}$$

**Step 4: Output voltage**

$$V_o = -4 + 18.6 = 14.6\text{ V}$$